

# Application Note

## Application Note

**Document No.: AN1111**

**APM32F103xB Hardware Development Guide**

**Version: V1.0**

# 1 Introduction

This application note is a minimum design specification for system hardware of the APM32F103xB series, including power supply scheme, clock source, reset mode, startup mode settings, and debugging management.

The detailed reference design drawing is also included in this document, including descriptions of main components, interfaces, and modes.

## Contents


<b>1</b>	<b>Introduction .....</b>	<b>1</b>
<b>2</b>	<b>Power supply.....</b>	<b>3</b>
2.1	Introduction .....	3
2.2	Power Supply Scheme .....	5
2.3	Power Management and Reset .....	6
<b>3</b>	<b>Clock .....</b>	<b>8</b>
3.1	External clock source.....	9
<b>4</b>	<b>Startup configuration .....</b>	<b>12</b>
<b>5</b>	<b>Debugging interface (SWJ-DP).....</b>	<b>13</b>
5.1	Debugging Pin Function Configuration .....	13
5.2	IO status during reset and just after reset .....	14
5.3	Recommended Debugging Interface Circuit.....	14
<b>6</b>	<b>Design Suggestions .....</b>	<b>17</b>
6.1	PCB Stacking.....	17
6.2	Power Supply Design .....	17
6.3	Clock Design.....	17
6.4	I/O Design .....	18
6.5	EMC and EMI.....	18
6.6	Grounding .....	18
6.7	Reference Schematic Diagram Design .....	19
<b>7</b>	<b>Revision history .....</b>	<b>20</b>

## 2 Power supply

### 2.1 Introduction

The power supply is the basis for stable operation of a system. The operating voltage is 2.0~3.6V. It can provide 1.6V power supply through the built-in voltage regulator. If the main power VDD is powered down, it can supply power to the backup power supply area through VBAT.

Figure 1 Power Supply Control Structure Block Diagram

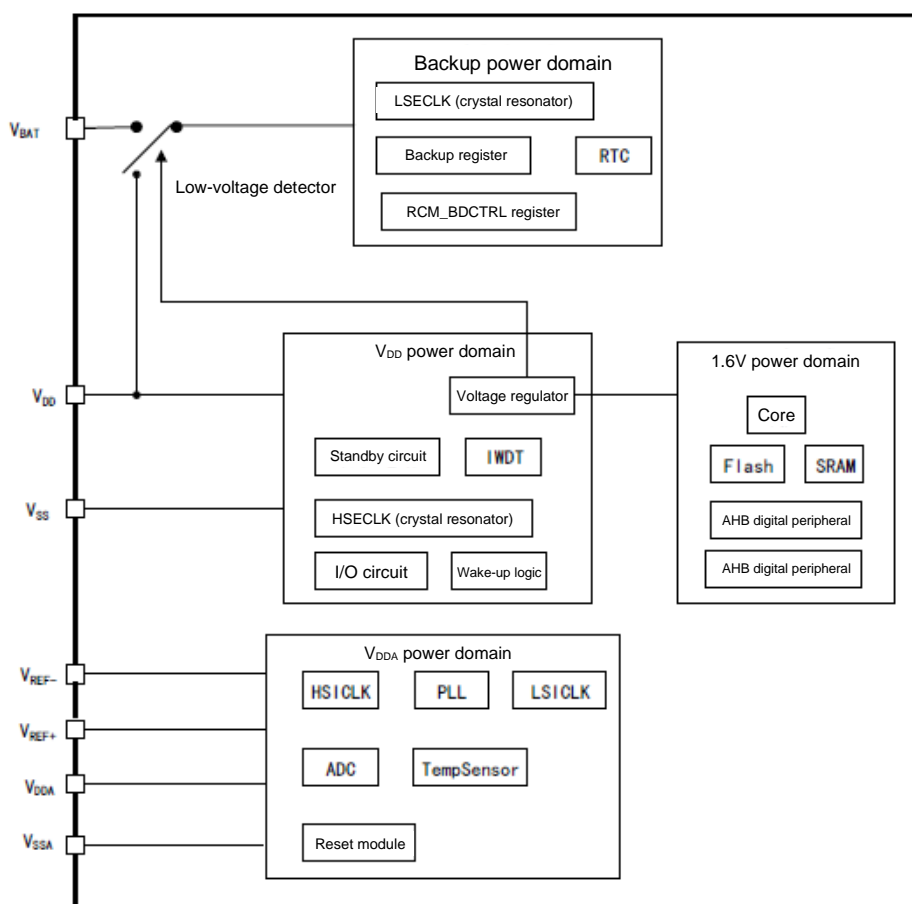

#### 2.1.1 Voltage regulator

Power can be supplied to 1.6V power domain in the following operating modes:

- Normal mode: In this mode, 1.6V power supply area runs at full power
- Stop mode: In this mode, 1.6V power supply area works in low-power state, all clocks are off, and peripherals stop work
- Standby mode: In this mode, 1.6V power supply area stops power supply, and except for the standby circuit, the content of register and SRAM will be lost.

### 2.1.2 Backup power field

- When VDD exists, the backup power supply area is powered by VDD. When VDD is powered down, the backup power supply area is powered by VBAT, which is used to save the content of backup register and maintain RTC function. Supply power to LSECLK crystal resonator, RTC, backup register, RCM\_BDCTRL register, PC13, PC14, and PC15.
- V<sub>BAT</sub> must be connected to V<sub>DD</sub> externally when no external battery is used.


### 2.1.3 Independent ADC power supply and reference voltage

Independent ADC power supply can improve the conversion accuracy, and the specific power pins are as follows:

- V<sub>DDA</sub>: Power pin of ADC
- V<sub>SSA</sub>: Independent power ground pin
- V<sub>REF+</sub> / V<sub>REF-</sub>: Reference voltage pin of ADC

## 2.2 Power Supply Scheme

Figure 2 Power Supply Scheme

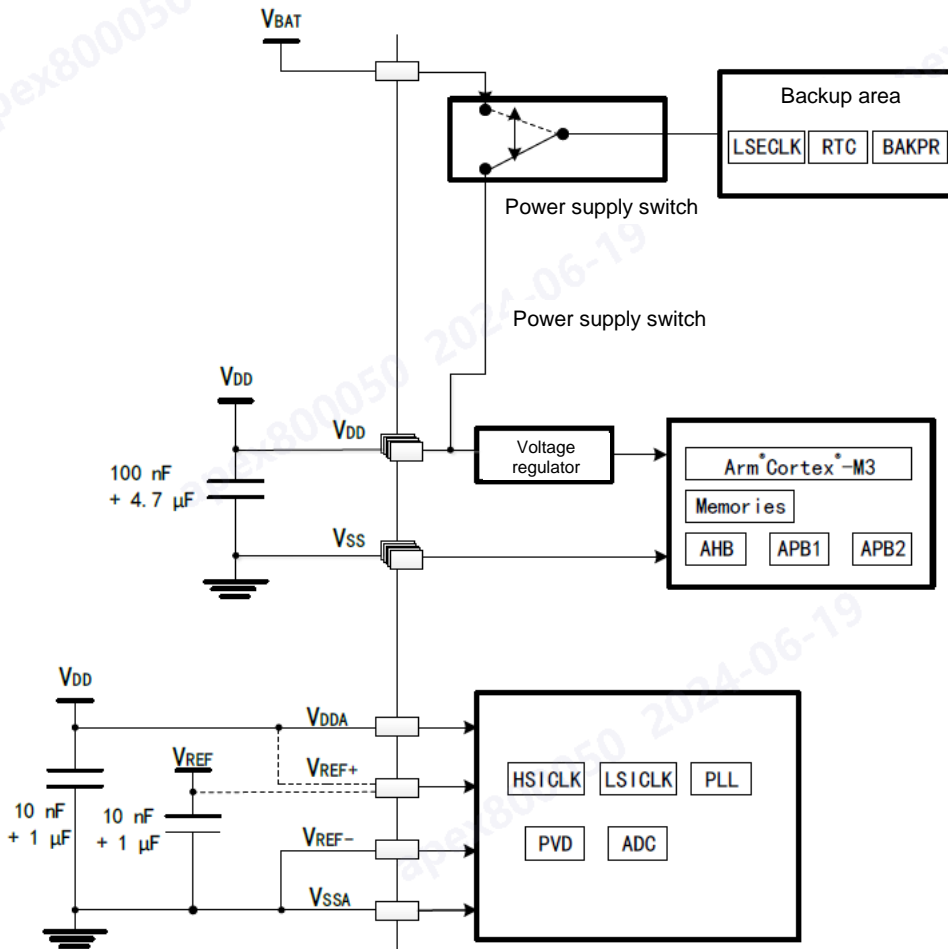

Pay attention to the power supply range of each power domain:

Table 1 Power Supply Scheme

Name	Voltage range	Description
V <sub>DD</sub>	2.0 ~ 3.6V	V <sub>DD</sub> powers IO interface directly, and powers the core circuit through the voltage regulator.
V <sub>DDA</sub>	2.4 ~ 3.6V	Connected to V <sub>DD</sub> to power the analog part of ADC, reset module, RC oscillator, and PLL. When ADC is used, V <sub>DDA</sub> is greater than or equal to 2.4V. V <sub>DDA</sub> and V <sub>VSSA</sub> must be connected to V <sub>DD</sub> and V <sub>VSS</sub> respectively.
V <sub>BAT</sub>	1.8V~3.6V	When V <sub>DD</sub> is turned off, it automatically powers the RTC, external 32.768KHz oscillator, and backup register.

Where:

Table 2 Precautions for Power Domain

$V_{DD}$	$V_{DD}$ must be connected to $V_{DD}$ power supply of an external capacitor (X 100nF ceramic capacitor(s) <sup>(1)</sup> and a tantalum capacitor not less than 4.7 $\mu$ F). $V_{DDX}$ represents that the number of $V_{DD}$ is x.
$V_{BAT}$	The $V_{BAT}$ pin can be connected to an external battery (1.8V<3.6V). If there is no external battery, an external 100nF ceramic capacitor <sup>(1)</sup> is required to be connected to the $V_{DD}$ power supply together.
$V_{DDA}$	The $V_{DDA}$ pin must be connected to an external capacitor (10nF ceramic capacitor <sup>(1)</sup> + 1 $\mu$ F tantalum capacitor).
$V_{REF+}$	The $V_{REF+}$ pin can be directly connected to $V_{DDA}$ or separately use an external reference voltage. A 10nF and a 1 $\mu$ F ceramic capacitor <sup>(1)</sup> must be connected to this pin. Meanwhile, the voltage range of $V_{REF+}$ must be between 2.4V and $V_{DDA}$ .


(1) It is recommended to use the ceramic capacitors made of X7R

## 2.3 Power Management and Reset

### 2.3.1 Power-on reset and power-down reset (POR and PDR)

When the  $V_{DD}/V_{DDA}$  is lower than the threshold voltage  $V_{POR}$  and  $V_{PDR}$ , the chip will automatically remain in the reset state. The waveform diagrams of power-on reset and power-down reset are as follows. For POR, PDR, hysteresis voltage and hysteresis time, please refer to the Datasheet.

Figure 3 Power-on Reset and Power-down Reset Oscillogram

 


### 2.3.2 Power Voltage Detector (PVD)

A threshold can be set for PVD to monitor whether  $v_{DD}/V_{DDA}$  is higher or lower than the threshold. If the interrupt is enabled, the interrupt can be triggered to process the  $V_{DD}/V_{DDA}$  exceeding the threshold in advance. The usage of PVD is as follows:

- (1) Set the PVDEN bit of the configuration register PMU\_CTRL to 1 to enable PVD

- (2) Select the voltage threshold of PVD through the PLSEL[2:0] bit of the configuration register PMU\_CTRL
- (3) The PVDOFLG bit of the configuration register PMU\_CSTS indicates whether the value of VDD is higher or lower than the threshold of PVD
- (4) When VDD/VDDA is detected to be below or above the PVD threshold, a PVD interrupt will be generated, and the threshold waveform is shown below. Please see the *Datasheet* for PVD threshold and hysteresis voltage.

Figure 4 PVD Threshold Oscillogram

 

### 2.3.3 System reset

The reset source is divided into external reset source and internal reset source.

Table 3 Reset Source

External reset source:	Low level on NRST pin.
Internal reset source:	<ol style="list-style-type: none"> <li>(1) Window watchdog termination count (WWDT reset)</li> <li>(2) Independent watchdog termination count (IWDT reset)</li> <li>(3) Software reset (SW reset)</li> <li>(4) Low-power management reset</li> <li>(5) Power reset</li> </ol>

A system reset will occur when any of the above events occurs. Besides, the reset event source can be identified by viewing the reset flag bit in RCM\_CSTS (control/status register).

#### 2.3.2.1 System reset circuit


The reset source is used in the NRST pin, which remains low in reset process. The internal reset source generates a pulse with a delay of at least 20 $\mu$ s on the NRST pin through the



pulse generator, which causes the NRST to maintain the level and generate reset; the external reset source directly pulls down the NRST pin level to generate reset.


**The system reset circuit is shown in Figure 5:**

Figure 5 System Reset Circuit

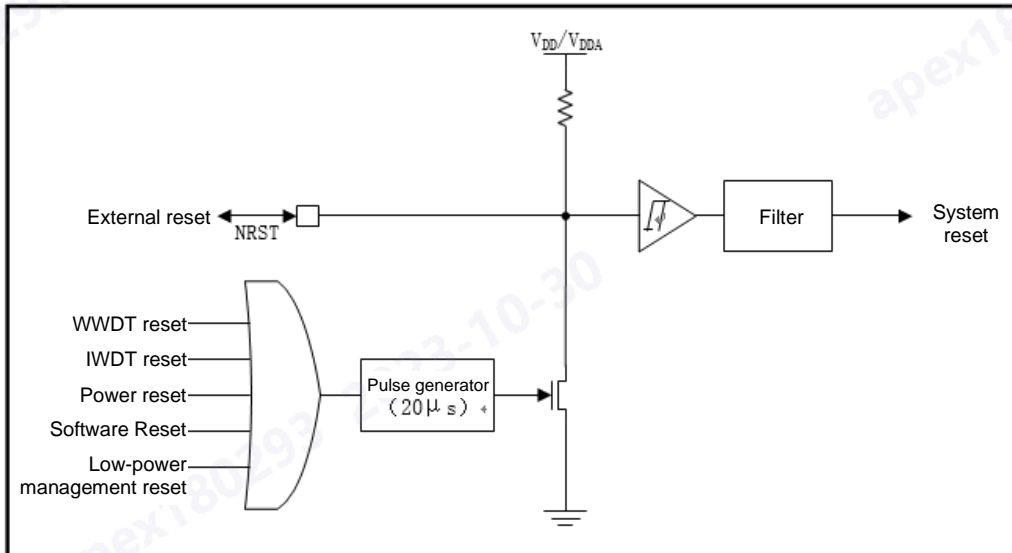

Recommend external reset circuit

Figure 6 External Reset Circuit

 


### 3 Clock

The clock sources of the whole system are: HSECLK, LSECLK, HSICLK, LSICLK and PLL. For the characteristics of the clock source, please refer to the relevant chapter of "Electrical Characteristics" in the datasheet.

**Clock tree:**

Figure 7 Clock Tree

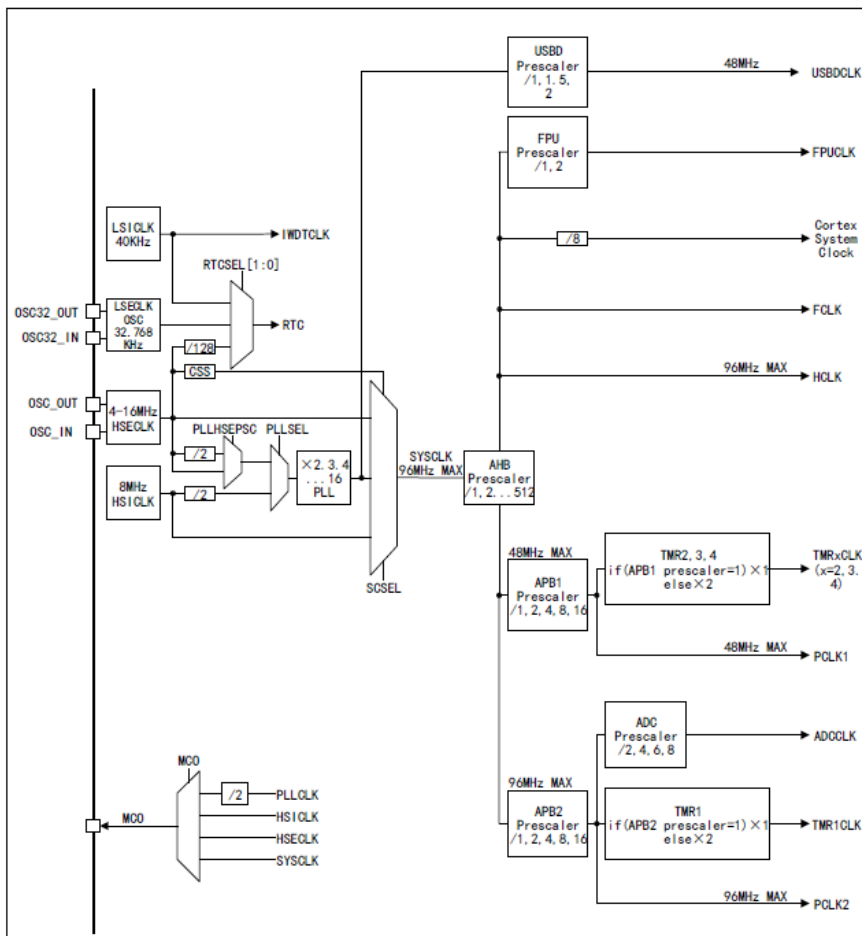

### 3.1 External clock source

The external clock signal includes HSECLK (high-speed external clock signal) and LSECLK (low-speed external clock signal).


There are two kinds of external clock sources:

- External clock of user
- External crystal/ceramic resonator

The hardware configuration of the two kinds of clock sources is shown in the figure below.

Figure 4 HSECLK/LSECLK Clock Source Hardware Configuration

Clock source	Hardware configuration
--------------	------------------------

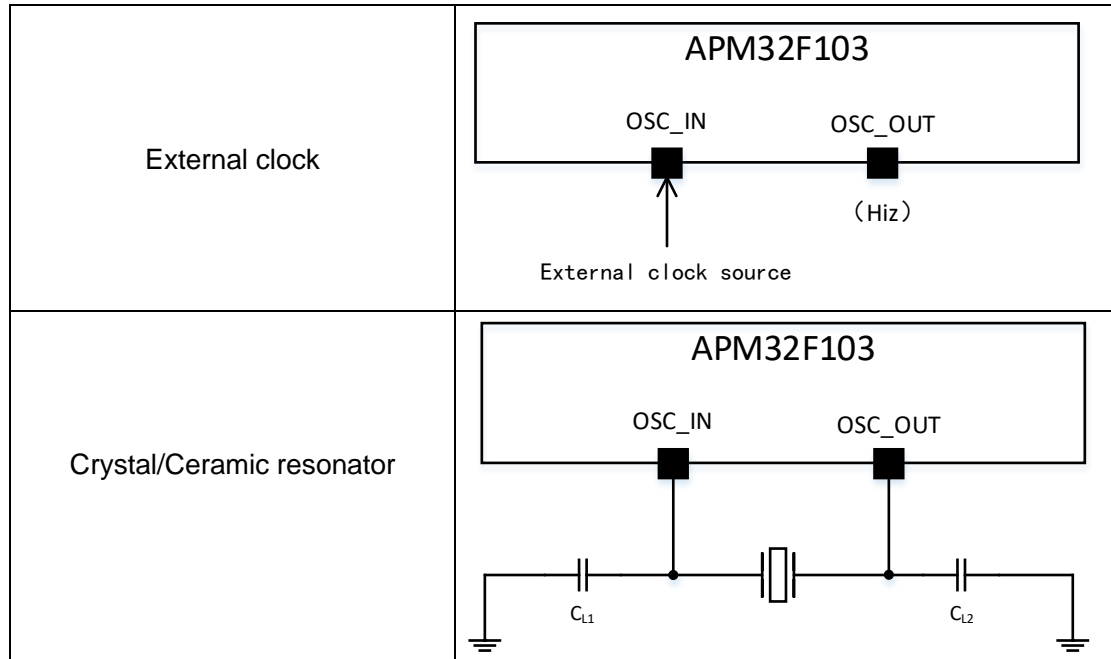

(1) In order to reduce the distortion of clock output and shorten the startup stabilization time, the crystal/ceramic resonator and load capacitor must be as close to the oscillator pin as possible. The value of the matching capacitance ( $C_{L1}$ ,  $C_{L2}$ ) must be adjusted according to the selected oscillator.

(2) The load capacitor  $C_L$  follows the formula of:  $C_L = C_{L1} \times C_{L2} / (C_{L1} + C_{L2}) + C_S$ .  $C_S$  is relevant capacitance of PCB and MCU pins. The typical value is between 2pF and 10pF.

### 3.1.1 HSECLK high-speed external clock signal

HSECLK clock signal is generated by two kinds of clock sources, i.e. HSECLK external crystal/ceramic resonator and HSECLK external clock .

Table 5 Clock Source Generating HSECLK

Name	Description
External clock source (HSECLK bypass)	Provide clock to the MCU through OSC_IN pin. The signal can be generated by ordinary function signal transmitter (in debugging), crystal oscillator and other signal generators; the waveform can be square wave, sine wave or triangle wave with 50% duty cycle, and the maximum frequency is up to 25MHz. In hardware connection, it must be connected to the OSC_IN pin and the OSC_OUT pin must be suspended.
Name	Description
External crystal/ceramic resonator (HSECLK crystal)	The clock is provided to MCU by the resonator, and the resonator includes crystal resonator and ceramic resonator. The frequency range is 4-16MHz. OSC_IN, OSC_OUT is required to connect the resonator,

	<p>and it can be turned on and off by setting the HSEEN bit in RCM_CTRL in the clock control register.</p> <p>Regarding the size of the external matching capacitor, please refer to the formula: <math>C_{L1} = C_{L2} = 2 * (C_L - C_s)</math>, where <math>C_s</math> is the stray capacitance of the PCB and MCU pins, and the typical value is 10pF. When selecting an external high-speed crystal resonator, it is recommended to select the one with a load capacitance of around 20pF, so that the external matching capacitors <sup>(1)</sup> <math>C_{L1}</math> and <math>C_{L2}</math> only need to have a capacitance value of 20pF, and the PCB should be as close as possible to the crystal oscillator pins.</p>
--	--

(1) It is recommended to use the temperature compensation capacitors made of NPO (COG) for the matching capacitor of the crystal oscillator.

### 3.1.2 LSECLK low-speed external clock signal

LSECLK clock signal is generated by two kinds of clock sources, i.e. LSECLK external crystal/ceramic resonator and LSECLK external clock .

Table 6 Clock Source Generating LSECLK

Name	Description
External clock source (LSECLK bypass)	<p>The clock is provided to MCU by OSC32_IN pin.</p> <p>The signal can be generated by ordinary function signal transmitter (in debugging), crystal oscillator and other signal generators; the waveform can be square wave, sine wave or triangle wave with 50% duty cycle, and the signal frequency needs to be 32.768kHz.</p> <p>For hardware connection, it must be connected to OSC32_IN pin, ensuring OSC32_OUT pin is suspended; for MCU configuration, the user can select this mode by setting LSEBCFG and LSEEN bits in RCM_BDCTRL (backup domain control register).</p>
External crystal/ceramic resonator (LSECLK crystal)	<p>The clock is provided to MCU by the resonator, and the resonator includes crystal resonator and ceramic resonator. The frequency is 32.768kHz.</p> <p>When needing to connect OSC32_IN and OSC32_OUT to the resonator, it can be turned on and off through the LSEEN bit in RCM_BDCTRL.</p> <p>Regarding the size of the external matching capacitor, please refer to the formula: <math>C_{L1} = C_{L2} = 2 * (C_L - C_s)</math>, where <math>C_s</math> is the stray capacitance of the PCB and MCU pins, and the typical value is 5pF. When selecting an external crystal resonator, it is recommended to select the one with a load capacitance of around 10pF, so that the external matching capacitors <sup>(1)</sup> <math>C_{L1}</math> and <math>C_{L2}</math> only need to have a capacitance value of 10pF, and the PCB should be as close as possible to the crystal</p>

oscillator pins during layout.
--------------------------------

(1) It is recommended to use the temperature compensation capacitors made of NPO or COG for the matching capacitor of the crystal oscillator.

## 4 Startup configuration

Since the CPU of Arm® Cortex®-M3 core obtains the reset vector from the ICode Bus (instruction bus), the startup can only start from the code area, and the typical one is Flash memory startup. However, APM32 MCU series realizes a special mechanism. By configuring the BOOT[1:0] pin parameter, there are three different startup modes, and the system can not only start from Flash memory or system memory, but also start from the built-in SRAM. The memory selected as the start zone is determined by the selected startup mode.


Table 7 Startup Mode Configuration and Access Mode

Startup mode selection pin		Startup mode	Access methods
BOOT0	BOOT1		
0	X	Main flash memory (Flash)	The main flash memory is mapped to the boot space, but it can still be accessed at its original address, that is, the contents of the flash memory can be accessed in two address areas.
1	0	System memory	The system memory is mapped to the boot space (0x00000000), but it can still be accessed at its original address.
1	1	Built-in SRAM	SRAM can be accessed only at the starting address.

- The user can select the startup mode after reset by setting the states of BOOT1 and BOOT0 pins.
- BOOT pin should keep the startup configuration required by user in standby mode. When exiting the standby mode, the value of boot pin will be latched.
- If you choose to start from built-in SRAM, you must use NVIC's exception table and offset register to remap the vector table to SRAM when writing the application code.

Recommended BOOT circuit design:

Figure 8 Recommended BOOT Circuit Design

 

## 5 Debugging interface (SWJ-DP)

The product supports serial debugging interface (SW-DP) and JTAG (JTAG-DP) debugging interface.

Table 8 Debugging Interface

SW-DP	SW-DP interface provides 2-pin (data + clock) interface for AHB module. Among them, some of 2 pins of SW-DP interface and 5 pins of JTAG interface are multiplexed.
JTAG	JTAG interface provides 5-pin standard JTAG interface for AHB access port.

### 5.1 Debugging Pin Function Configuration

- Realize the on-line programming and debugging of the chip.
- Use KEIL/IAR and other software to implement on-line debugging, downloading and programming.
- Flexible implementation of production of bus-off programmer.

Table 9 Pin Function Configuration

SWJ- CFG[2:0]	Configured as dedicated pin for debugging	I/O port assignment of SWJ interface				
		PA13/ JTMS/ SWDIO	PA14/ JTCK/ SWCLK	PA15/ JTDI	PB3/ JTDO	PB4/ JNTRST
Others	Disable	Release				
100	Both JTAG-DP interface and SW-DP interface are disabled					

	Disable					
010	JTAG-DP interface is disabled, and SW-DP interface is enabled	Special	Special	Release		
001	All SWJ pins (JTAG-DP+SW-DP) Except JNTRST pin	Special	Special	Special	Special	Release
000	All SWJ pins (JTAG-DP+SW-DP) Reset state	Special	Special	Special	Special	Special

## 5.2 IO status during reset and just after reset


If the multiplexing function is not enabled during and just after GPIO reset, the I/O port will be configured as floating input mode, and in such case, the pull-up/pull-down resistor is disabled in input mode. After reset, the JTAG pin is put in the input pull-up or pull-down mode, and the specific configuration is as follows:

- PA15: JTDI is set to pull-up mode;
- PA14: JTCK is set to pull-down mode;
- PA13: JTMS in pull-up mode
- PB4: JNTRST is set to pull-up mode;
- PB3: JTDO is in floating mode.

## 5.3 Recommended Debugging Interface Circuit

Recommended JTAG interface reference design:

Figure 9 JTAG Interface Circuit

 


## Note:

(1) The JTAG interface reference design is to add an external pull-up resistor to the JTMS, JTDI, JTDO, and NJTRST pins, and add a pull-down resistor to the JTCK pin, which can enhance the anti-interference capability of downloading and debugging. If these pins are multiplexed for other functions, please evaluate the impact of pull-up and pull-down resistors and make adjustments based on the actual situation.

Recommended SWD interface reference design:



Figure 10 SWD Interface Circuit

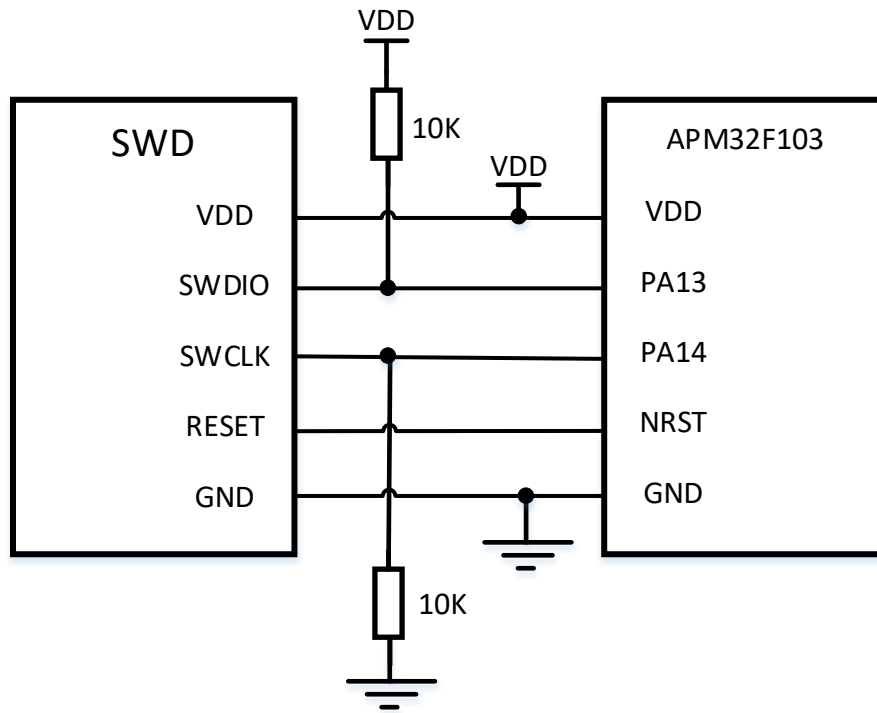**Note:**

(1) The reference design for the SWD interface is to add an external pull-up resistor and pull-down resistor to the SWDIO and SWCLK pins, which can enhance the anti-interference ability of downloading and debugging. If these two pins are multiplexed for other functions, please evaluate the impact of the pull-up and pull-down resistors and make adjustments according to the actual situation.

## 6 Design Suggestions


### 6.1 PCB Stacking

- Number of layers: It is recommended to use the multi-layer design to ensure independent GND and power layers, which can better ensure signal integrity and enhance shielding effect. However, considering the costs, users can reduce the number of stacking layers while ensuring good grounding and power supply.
- Signal and formation: The signal layer should be adjacent to the formation. This helps to reduce the electromagnetic interference and the loop area of the signal path, and can serve as a reference plane for the signal.
- Power supply and formation: The power supply layer should be separated from the formation.

### 6.2 Power Supply Design

- Stable power input: Ensure stable power supply and filter the power noise.
- Decoupling capacitors: Place one or more 100nF decoupling capacitors at each VDD pin near the chip.

Figure 11 Recommended Power Pin Decoupling Capacitor Layout Design

 

- Power supply wiring: It is recommended that the power supply wiring should be wide and short enough to reduce the influence of parasitic parameters and the voltage drop.


### 6.3 Clock Design

- Crystal oscillator selection: Choose an appropriate crystal oscillator and ensure it meets the operating frequency and stability requirements of the MCU.
- Wiring suggestions: Clock signal wiring should be as short as possible and be away from strong interference signals such as high current and high-speed signal

lines. It is recommended to use package processing to enhance the shielding effect.

- Layout suggestions: The crystal oscillator circuit should be placed close to the chip, and to reduce the interference, it is best to ensure a complete ground plane below the entire crystal oscillator circuit.

Figure 12 Recommended Clock Pin Layout Design

 

## 6.4 I/O Design

- I/O configuration: Correctly configure the modes of I/O ports, such as input, output, pull-up and pull-down, and open-drain mode.
- Protection: For externally connected I/O ports, consider adding the voltage protection (TVS tube) and series resistor.

## 6.5 EMC and EMI

- Layout: Consider the design of electromagnetic compatibility (EMC) and electromagnetic interference (EMI), and the layout should be reasonable. For example, keep the MCU away from high-power and strong interference sources, and consider how to reduce the loop area, etc.
- Shielding: Use shielding and reasonable grounding strategies for sensitive and high-speed circuits.


## 6.6 Grounding

- Single-point grounding: In low-frequency circuits or circuits with not high noise requirements, adopting single-point grounding can avoid formation of ground loop. In such case, all grounding points should be connected to a common grounding point, which is usually the negative pole of the power supply or some grounding plane on the circuit board.

- Multi-point grounding: In high-frequency circuits or high-current circuits, usually multi-point grounding is used. The grounding of each component or function module is directly connected to the nearest grounding plane, which can reduce the impedance of the ground wire, and reduce the noise and electromagnetic interference.
- Separation of analog from digital ground: If the MCU processes the analog and digital signals simultaneously, the analog ground and digital ground should be processed separately. This can be achieved by physically separating two ground planes and merging them at a certain point to connect them to the main ground, which can reduce the interference of digital noise with the analog signals.

## 6.7 Reference Schematic Diagram Design

Figure 13 Reference Schematic Diagram

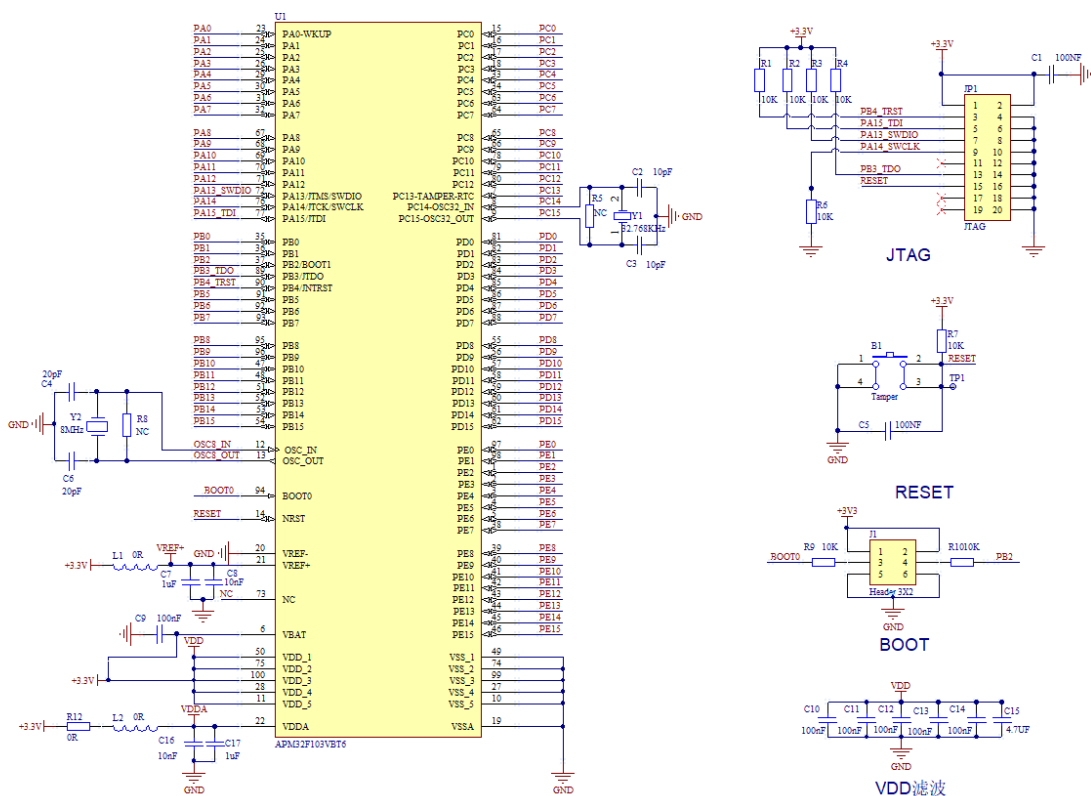

## 7 Revision history

Table 10 Document Revision History

Date	Version	Revision History
June, 2024	V1.0	New edition

## Statement

This document is formulated and published by Geehy Semiconductor Co., Ltd. (hereinafter referred to as “Geehy”). The contents in this document are protected by laws and regulations of trademark, copyright and software copyright. Geehy reserves the right to make corrections and modifications to this document at any time. Read this document carefully before using Geehy products. Once you use the Geehy product, it means that you (hereinafter referred to as the “users”) have known and accepted all the contents of this document. Users shall use the Geehy product in accordance with relevant laws and regulations and the requirements of this document.

### 1. Ownership

This document can only be used in connection with the corresponding chip products or software products provided by Geehy. Without the prior permission of Geehy, no unit or individual may copy, transcribe, modify, edit or disseminate all or part of the contents of this document for any reason or in any form.

The “极海” or “Geehy” words or graphics with “®” or “™” in this document are trademarks of Geehy. Other product or service names displayed on Geehy products are the property of their respective owners.

### 2. No Intellectual Property License

Geehy owns all rights, ownership and intellectual property rights involved in this document.

Geehy shall not be deemed to grant the license or right of any intellectual property to users explicitly or implicitly due to the sale or distribution of Geehy products or this document.

If any third party’s products, services or intellectual property are involved in this document, it shall not be deemed that Geehy authorizes users to use the aforesaid third party’s products, services or intellectual property. Any information regarding the application of the product, Geehy hereby disclaims any and all warranties and liabilities of any kind, including without limitation warranties of non-infringement of intellectual property rights of any third party, unless otherwise agreed in sales order or sales contract.

### 3. Version Update

Users can obtain the latest document of the corresponding models when ordering Geehy products.

If the contents in this document are inconsistent with Geehy products, the agreement in the sales order or the sales contract shall prevail.

### 4. Information Reliability

The relevant data in this document are obtained from batch test by Geehy Laboratory or cooperative third-party testing organization. However, clerical errors in correction or errors caused by differences in testing environment may occur inevitably. Therefore, users should understand that Geehy does not bear any responsibility for such errors that may occur in this document. The relevant data in this document are only used to guide users as performance parameter reference and do not constitute Geehy's guarantee for any product performance.

Users shall select appropriate Geehy products according to their own needs, and effectively verify and test the applicability of Geehy products to confirm that Geehy products meet their own needs, corresponding standards, safety or other reliability requirements. If losses are caused to users due to user's failure to fully verify and test Geehy products, Geehy will not bear any responsibility.

### 5. Legality

USERS SHALL ABIDE BY ALL APPLICABLE LOCAL LAWS AND REGULATIONS WHEN USING THIS DOCUMENT AND THE MATCHING GEEHY PRODUCTS. USERS SHALL UNDERSTAND THAT THE PRODUCTS MAY BE RESTRICTED BY THE EXPORT, RE-EXPORT OR OTHER LAWS OF THE COUNTRIES OF THE PRODUCTS SUPPLIERS, GEEHY, GEEHY DISTRIBUTORS AND USERS. USERS (ON BEHALF OR ITSELF, SUBSIDIARIES AND AFFILIATED ENTERPRISES) SHALL AGREE AND PROMISE TO ABIDE BY ALL APPLICABLE LAWS AND REGULATIONS ON THE EXPORT AND RE-EXPORT OF GEEHY PRODUCTS AND/OR TECHNOLOGIES AND DIRECT PRODUCTS.

### 6. Disclaimer of Warranty

THIS DOCUMENT IS PROVIDED BY GEEHY "AS IS" AND THERE IS NO WARRANTY OF ANY KIND, EITHER EXPRESSED OR IMPLIED, INCLUDING, BUT NOT

LIMITED TO, THE WARRANTIES OF MERCHANTABILITY AND FITNESS FOR A PARTICULAR PURPOSE, TO THE EXTENT PERMITTED BY APPLICABLE LAW.

GEEHY'S PRODUCTS ARE NOT DESIGNED, AUTHORIZED, OR WARRANTED FOR USE AS CRITICAL COMPONENTS IN MILITARY, LIFE-SUPPORT, POLLUTION CONTROL, OR HAZARDOUS SUBSTANCES MANAGEMENT SYSTEMS, NOR WHERE FAILURE COULD RESULT IN INJURY, DEATH, PROPERTY OR ENVIRONMENTAL DAMAGE.

IF THE PRODUCT IS NOT LABELED AS "AUTOMOTIVE GRADE," IT SHOULD NOT BE CONSIDERED SUITABLE FOR AUTOMOTIVE APPLICATIONS. GEEHY ASSUMES NO LIABILITY FOR THE USE BEYOND ITS SPECIFICATIONS OR GUIDELINES.

THE USER SHOULD ENSURE THAT THE APPLICATION OF THE PRODUCTS COMPLIES WITH ALL RELEVANT STANDARDS, INCLUDING BUT NOT LIMITED TO SAFETY, INFORMATION SECURITY, AND ENVIRONMENTAL REQUIREMENTS. THE USER ASSUMES FULL RESPONSIBILITY FOR THE SELECTION AND USE OF GEEHY PRODUCTS. GEEHY WILL BEAR NO RESPONSIBILITY FOR ANY DISPUTES ARISING FROM THE SUBSEQUENT DESIGN OR USE BY USERS.

#### 7. Limitation of Liability

IN NO EVENT, UNLESS REQUIRED BY APPLICABLE LAW OR AGREED TO IN WRITING WILL GEEHY OR ANY OTHER PARTY WHO PROVIDES THE DOCUMENT AND PRODUCTS "AS IS", BE LIABLE FOR DAMAGES, INCLUDING ANY GENERAL, SPECIAL, DIRECT, INCIDENTAL OR CONSEQUENTIAL DAMAGES ARISING OUT OF THE USE OR INABILITY TO USE THE DOCUMENT AND PRODUCTS (INCLUDING BUT NOT LIMITED TO LOSSES OF DATA OR DATA BEING RENDERED INACCURATE OR LOSSES SUSTAINED BY USERS OR THIRD PARTIES). THIS COVERS POTENTIAL DAMAGES TO PERSONAL SAFETY, PROPERTY, OR THE ENVIRONMENT, FOR WHICH GEEHY WILL NOT BE RESPONSIBLE.

#### 8. Scope of Application

The information in this document replaces the information provided in all previous versions of the document.

© 2024 Geehy Semiconductor Co., Ltd. - All Rights Reserved